

BASIC ELECTRONICS ASSIGNMENT

Submitted by
Muhammad Ahsan Akbar

Cms : 284918


Section : BESE-10A

Index

Question #	Page #
Q#1	1
Q#2	4
Q # 3	5
Q # 4	7
Q # 5	10

①

Question - 1

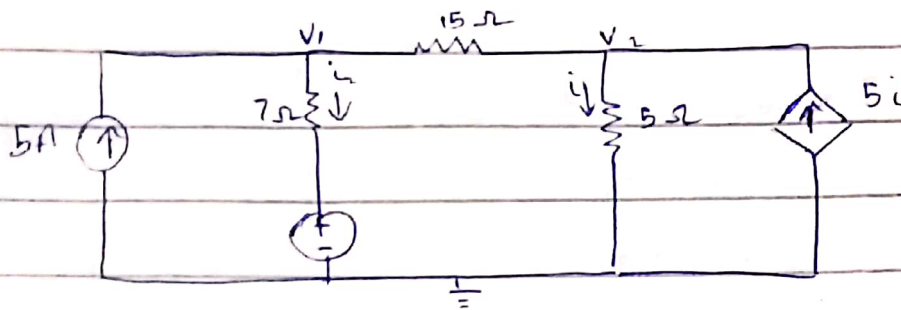


We will apply Superposition theorem
First we will only consider current source
of 5A & ignore voltage source

At node V_1' :-

$$I_1 + I_2 + I_3 = 0$$
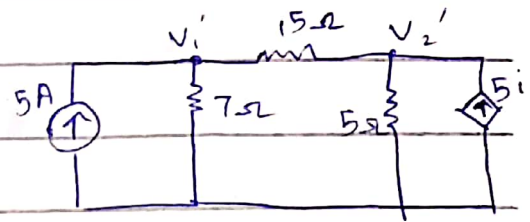
$$-5 + \frac{V_1' - 0}{7} + \frac{V_1' - V_2'}{15} = 0$$



$$\frac{-525}{105} + 15V_1' + 7V_1' - 7V_2' = 0$$

$$22V_1' - 7V_2' - 525 = 0 \quad (i)$$

At node V_2' :-

$$-5 + \frac{V_2'}{5} + \frac{V_2' - V_1'}{15} = 0 \quad (ii)$$

As $i = \frac{V_2'}{5}$ put in (ii)

$$-5 \left(\frac{V_2'}{5} \right) + \frac{V_2'}{5} + \frac{V_2' - V_1'}{15} = 0$$

$$\frac{-15V_2' + 3V_2' + V_2' - V_1'}{15} = 0$$

2

$$-11v_2' - v_1' = 0 \quad \text{---(i)}$$

Put in (i)

$$-242v_2' - 7v_2' - 525 = 0$$

$$-249v_2' - 525 = 0$$

$$v_2' = -21084 \text{ V}$$

Put in (ii)

$$-11(-21084) - v_1' = 0$$


$$v_1' = 231924 \text{ V}$$

Now, consider only voltage source
i.e. ignore current source

At node v_1'' :-

$$I_1 + I_2 + I_3 = 0$$
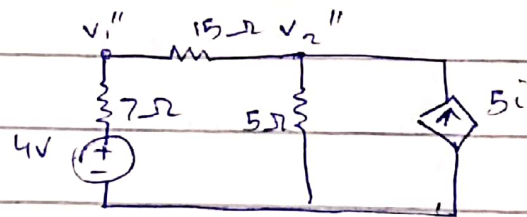
$$\frac{v_1'' - 4}{7} + \frac{v_1'' - v_2''}{15} = 0$$



$$15v_1'' - 60 + 7v_1'' - 7v_2'' = 0$$

$$22v_1'' - 7v_2'' - 60 = 0 \quad \text{---(iii)}$$

At node v_2'' :-

$$I_1 + I_2 + I_3 = 0$$

$$-5i + \frac{v_2''}{5} + \frac{v_2'' - v_1''}{15} = 0$$

$$v_1'' = -11v_2'' \quad \text{---(iv) put in (iii)}$$

$$-242v_2'' - 7v_2'' - 60 = 0$$

$$v_2'' = -0.2409 \text{ V}$$

put in (iv)

③

$$v_1'' = -11 (-0.2409)$$

$$v_1'' = 2.6506$$

Add v_1' & v_1'' to get v_1'

$$v_1 = v_1' + v_1''$$

$$= 23.1924 + 2.6506$$

$$v_1 = 25.8430 \text{ V}$$

Add v_1' & v_2'' to get v_2

$$v_2 = v_1' + v_2''$$

$$= -2.1084 - 0.2409$$

$$v_2 = -2.3493 \text{ V}$$

For i_1 :-

$$i = \frac{v_2}{5} = \frac{-2.3493}{5}$$


$$i = -0.46986$$

For i_2 :-


$$i_2 = \frac{v_1 - 4}{7} = \frac{25.8430 - 4}{7}$$

$$i_2 = 3.1204 \text{ A}$$

Question - 2

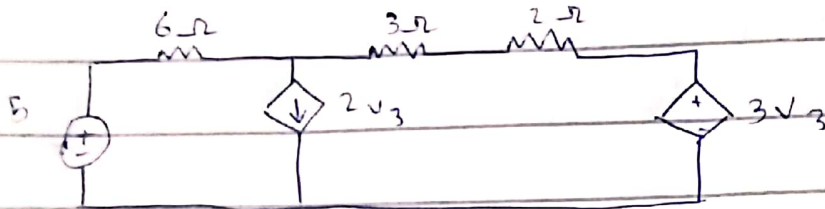

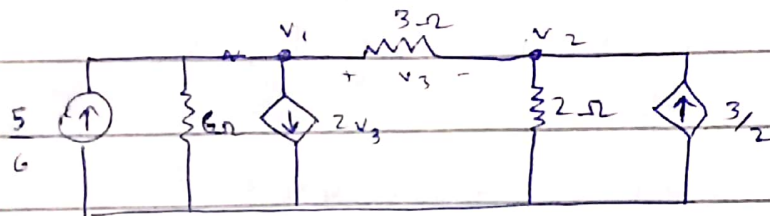Converting voltage sources to current sources



At node v_1 :-

$$-\frac{5}{6} + \frac{v_1}{6} + 2v_3 + \frac{v_1 - v_2}{3} = 0$$

$$-5 + v_1 + 12v_3 + 2v_1 - 2v_2 = 0$$

$$-5 + v_1 + 12v_3 + 2v_1 - 2v_2 = 0 \quad \boxed{\therefore v_3 = v_1 - v_2}$$

$$15v_1 - 14v_2 - 5 = 0 \quad \text{--- (1)}$$

At node v_2 :-

$$-\frac{3}{2}v_3 + \frac{v_2}{2} + \frac{v_2 - v_1}{3} = 0$$

$$-9v_3 + 3v_2 + 2v_2 - 2v_1 = 0$$

$$\therefore v_3 = v_1 - v_2$$

$$-9v_1 + 9v_2 + 3v_2 + 2v_2 - 2v_1 = 0$$

$$-11v_1 + 14v_2 = 0$$

$$v_2 = \frac{11}{14}v_1 \quad \text{--- (2)}$$

;

5

put v_2 in ①

$$15v_1 - 14\left(\frac{11}{14}v_1\right) - 5 = 0$$

$$15v_1 - 11v_1 - 5 = 0$$

$$4v_1 = 5$$

$$v_1 = \frac{5}{4} = 1.25$$

put v_1 in ②

$$v_2 = \frac{11}{14} \times \frac{5}{4}$$


$$v_2 = 0.9821$$

$$\text{as } v_3 = v_1 - v_2$$


$$v_3 = 1.25 - 0.9821$$

$$v_3 = 0.2679$$

Question - 3

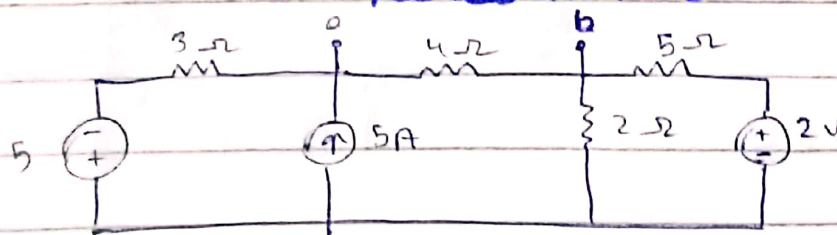

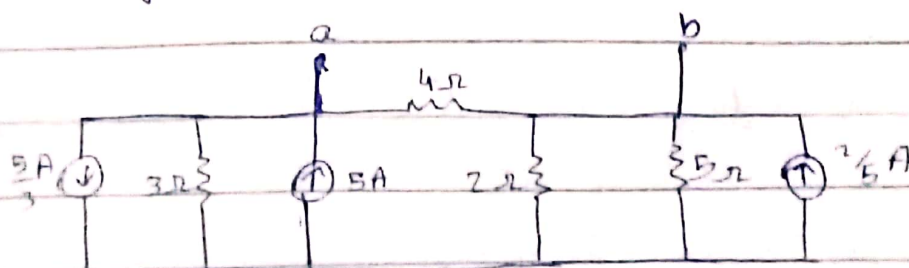Converting voltage sources to current sources



(6)


Combining $5A$ & $5/3 A$ currents

$$I = 5 - \frac{5}{3} = \frac{10}{3} A$$

Combining 5Ω & 2Ω resistors

$$R = \frac{5 \times 2}{5 + 2} = \frac{10}{7} \Omega$$

Modified circuit is

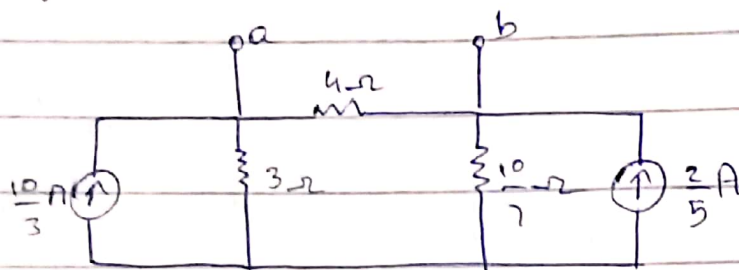


Apply Norton's Theorem

For I_{ab} :-

$$I_{ab} \left(3 + \frac{10}{7} \right) - \frac{10}{3} \times 3 + \frac{10}{7} \times \frac{2}{5} = 0$$

$$I_{ab} \left(\frac{31}{7} \right) - 10 + \frac{4}{7} = 0$$
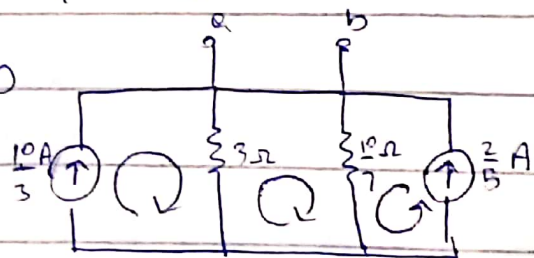
$$I_{ab} = \frac{66}{7} \times \frac{7}{31}$$



$$I_{ab} = 2.1290 A$$

For equivalent resistance


$$R_m = 4 \parallel \left(3 + \frac{10}{7} \right)$$

$$= 4 \parallel \frac{31}{7}$$

7

$$R_m = 2.1017 \Omega$$

For 10Ω resistor Norton's circuit is

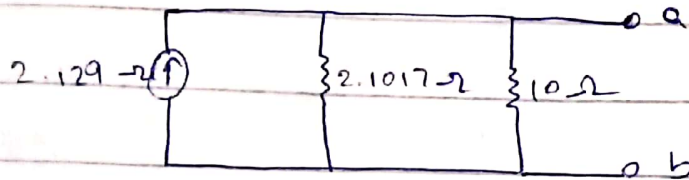

For current across 10Ω resistor

$$I_{10} = \frac{2.1017}{2.1017 + 10} \times 2.1290$$

$$I = 0.3697 \text{ A}$$


For Power absorbed

$$P = I^2 R$$

$$= (0.3697)^2 \times 10$$

$$P = 1.3697 \text{ W}$$

Question - 4

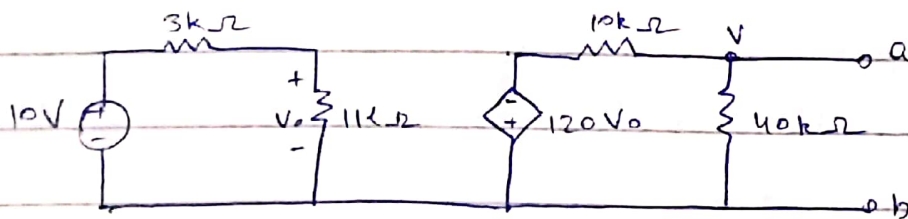

Part (a) :-

For V_0 :-

Apply voltage divider rule

$$V_0 = 10 \times \frac{1}{1 + 3}$$

$$V_0 = \frac{5}{2} \text{ V} = 2.5 \text{ V}$$

At node V :-

$$I_1 + I_2 = 0$$

$$\frac{V - 120V_0}{10000} + \frac{V}{40000} = 0 \quad \text{--- (1)}$$

put value of V_0 in (1)

$$\frac{V - 120\left(\frac{5}{2}\right)}{10000} + \frac{V}{40000} = 0$$

$$\frac{V - 300}{10000} + \frac{V}{40000} = 0$$

$$\frac{4V - 1200}{40000} = 0$$

$$5V - 1200 = 0$$

$$V = \frac{1200}{5}$$

$$\boxed{V = 240V}$$

For short circuit :-

$$I = \frac{120 \times \frac{5}{2}}{10000}$$

$$I = \frac{300}{10000} = \frac{3}{100}$$

For R_{TH}


$$R_{TH} = \frac{V}{I} = \frac{240}{0.03}$$

$$\boxed{R_{TH} = 8k\Omega}$$

9

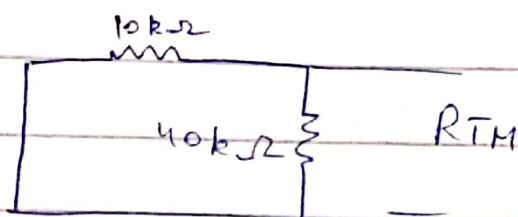Part (b) :-

We will remove 10V independent voltage source, Due to this ' v_o ' has zero voltage, As dependent voltage source is equal to $120v_o$ so it also becomes zero. Final circuit is



For R_{TH} :

$$R_{TH} = \frac{40000 \times 10000}{40000 + 10000}$$


$$= \frac{400000000}{50000}$$

$$R_{TH} = 8000 \Omega$$

$$R_{TH} = 8K \Omega$$

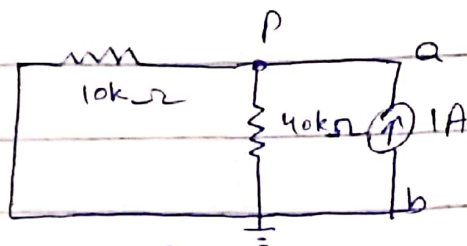Part (c) :-

As all independent sources are set to zero so v_o is also zero due to which dependent source has no effect we will attach 1A current b/w c & e b. Final circuit will be as shown



At point P :-

$$\frac{P}{10k} + \frac{P}{40k} = 1$$

$$\frac{4P + P}{40k} = 1$$


$$P = \frac{40k}{5} = 8kV$$

For R_{TH} :-

$$R_{TH} = \frac{P}{I} = \frac{8kV}{1A}$$

$$R_{TH} = 8k\Omega$$

Question - 5

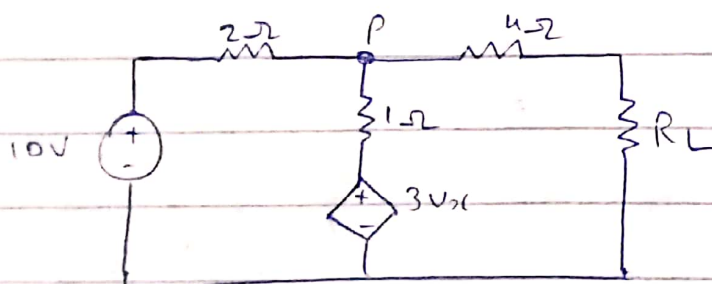

We have to find maximum power for load R_L . As we know

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

So we will find V_{TH} & R_{TH} by R_L

For R_{TH} , we will replace R_L by $1V$ voltage source & ignore $10V$ independent voltage source, Modified circuit will be

Apply mesh analysis

It is clear that

$$V_x = 2I_1$$

For mesh 1

$$3I_1 + 3V_x - I_2 = 0$$

$$3I_1 + 3(2I_1) - I_2 = 0$$

$$9I_1 - I_2 = 0$$

$$I_2 = 9I_1 \quad \text{--- (1)}$$

For mesh 2 :

$$5I_2 + 1 - 3V_x - I_1 = 0$$

$$5I_2 + 1 - 3(2I_1) - I_1 = 0$$

$$5I_2 + 1 - 7I_1 = 0$$

From eq (1) $I_2 = 9I_1$

$$5(9I_1) + 1 - 7I_1 = 0$$


$$I_1 = -0.0263$$

$$I_2 = -0.2368$$

For R_{TH}

$$R_{TH} = \frac{V}{I_2} = \frac{1}{0.2368} = 4.22 \Omega$$

$$R_{TH} = 4.22 \Omega$$

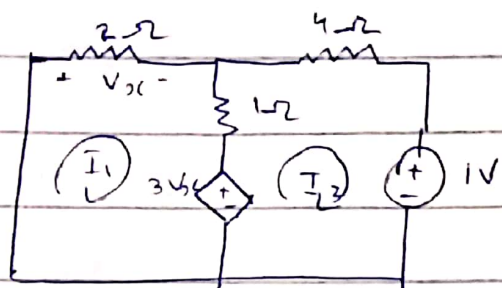

For circuit in mesh 1

$$-10 + 3I_1 + 3V_x = 0$$

$$-10 + 3I_1 + 3(2I_1) = 0$$

$$9I_1 = 10$$

$$I_1 = \frac{10}{9} = 1.11 \text{ A}$$

As $V_{oc} = 10 - P$

$$I_1 = \frac{V_{oc}}{R_{2\Omega}}$$

$$1.11 = \frac{10 - P}{2}$$

$$P = 7.78 \text{ V}$$

For P_{max} :-

$$P_{max} = \frac{V_{TH}^2}{R_{TH}}$$

$$= \frac{(7.78)^2}{4 \times 4.22}$$

$$P_{max} = 3.5858 \text{ W}$$